

## Homework 6 – DSD2

### Exercise 1

	0	20,000	40,000	60,000
w[3:0]	1	2	4	8
y[1:0]	0	1	2	3
w[3:0]	1	2	4	8
y[1:0]	0	1	2	3

library ieee;

use ieee.std\_logic\_1164.all;

entity Hw6Q1PriorityEncoder is

port (

w : in std\_logic\_vector (3 downto 0);

y : out std\_logic\_vector (1 downto 0)

);

end entity Hw6Q1PriorityEncoder;

architecture obehavior of Hw6Q1PriorityEncoder is

begin

if\_proc : process(w) is begin

if w = "0001" then

y <= "00";

elsif w = "0010" then

y <= "01";

elsif w = "0100" then

y <= "10";

else


y <= "11";

end if;

end process;

end obehavior;

### Exercise 2

 

```

library ieee;
use ieee.std_logic_1164.all;

entity Hw6Q2PriorityEncoder is
    port (
        w : in std_logic_vector(7 downto 0);
        y : out std_logic_vector(2 downto 0)
    );
end Hw6Q2PriorityEncoder;

architecture Behavioral of Hw6Q2PriorityEncoder is
begin
    case_proc : process(w) is begin
        case w is
            when "00000001" => y <= "000";
            when "00000010" => y <= "001";
            when "00000100" => y <= "010";
            when "00001000" => y <= "011";
            when "00010000" => y <= "100";
            when "00100000" => y <= "101";
            when "01000000" => y <= "110";
            when others => y <= "111";
        end case;
    end process case_proc;
end Behavioral;

```

```

library ieee;
use ieee.std_logic_1164.all;
use IEEE.NUMERIC_STD.ALL;

```

```

entity Hw6Q2PriorityEncoderTB is
end Hw6Q2PriorityEncoderTB;

```

```

architecture tb of Hw6Q2PriorityEncoderTB is
    signal w : std_logic_vector(7 downto 0);
    signal y : std_logic_vector(2 downto 0);

```

```

begin
    dut : entity work.Hw6Q2PriorityEncoder
    port map (
        w => w, y => y
    );

```

```

stimuli : process
    -- use the unsigned type when doing math, requires numericstd library
    variable test_vector: unsigned(7 downto 0) := "00000001";
    variable test_result: unsigned(2 downto 0) := "000";

```


```

begin
  for i in 0 to 7 loop
    -- variables can be assigned to signals
    -- unsigned is simply converted to std_logic_vector
    w <= std_logic_vector(test_vector);
    wait for 10 ns;
    test_vector := shift_left(test_vector, 1);


    assert y = std_logic_vector(test_result)
    report "error, expected y = " & to_hstring(test_result) &
    "actual value is = " & to_hstring(y);
    test_result := test_result + 1;
    wait for 10 ns;
  end loop;
  wait;
end process;
end tb;

```


### Exercise 3

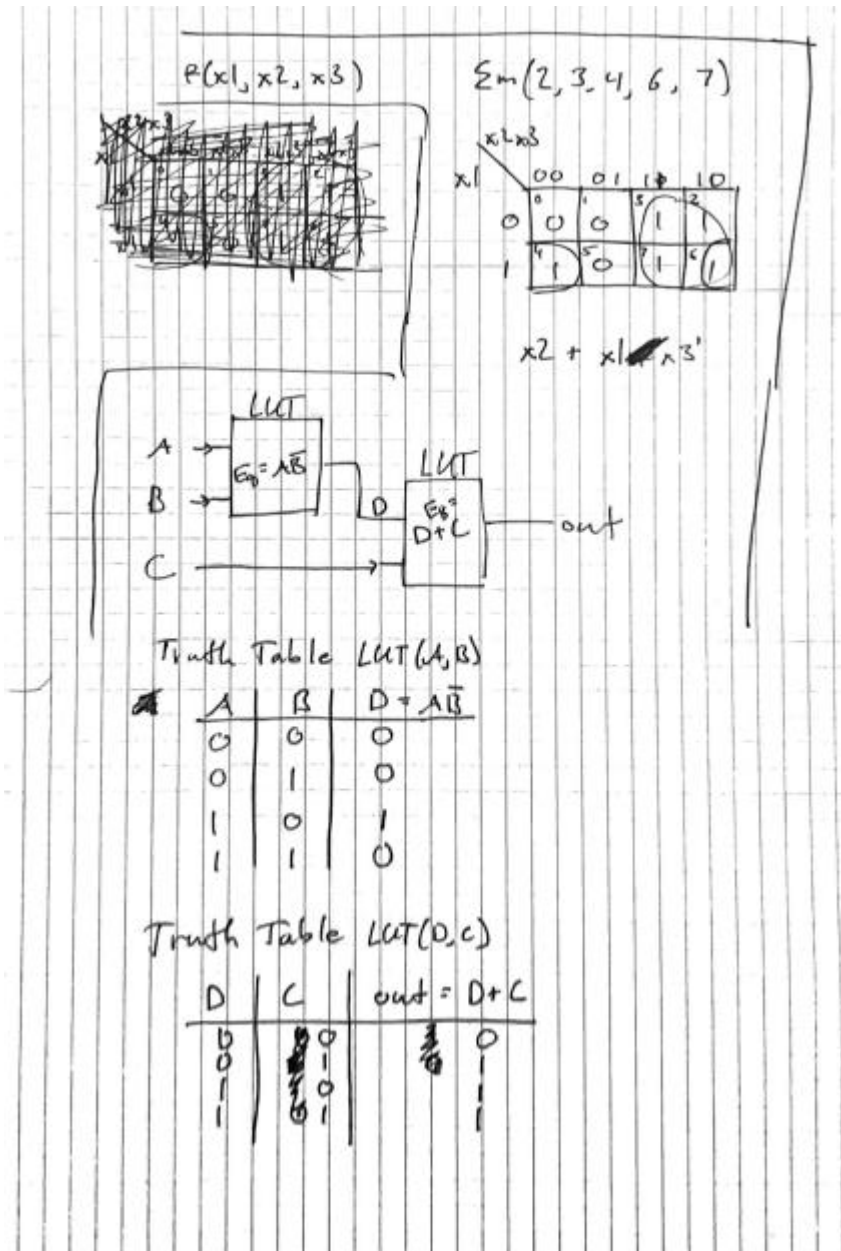
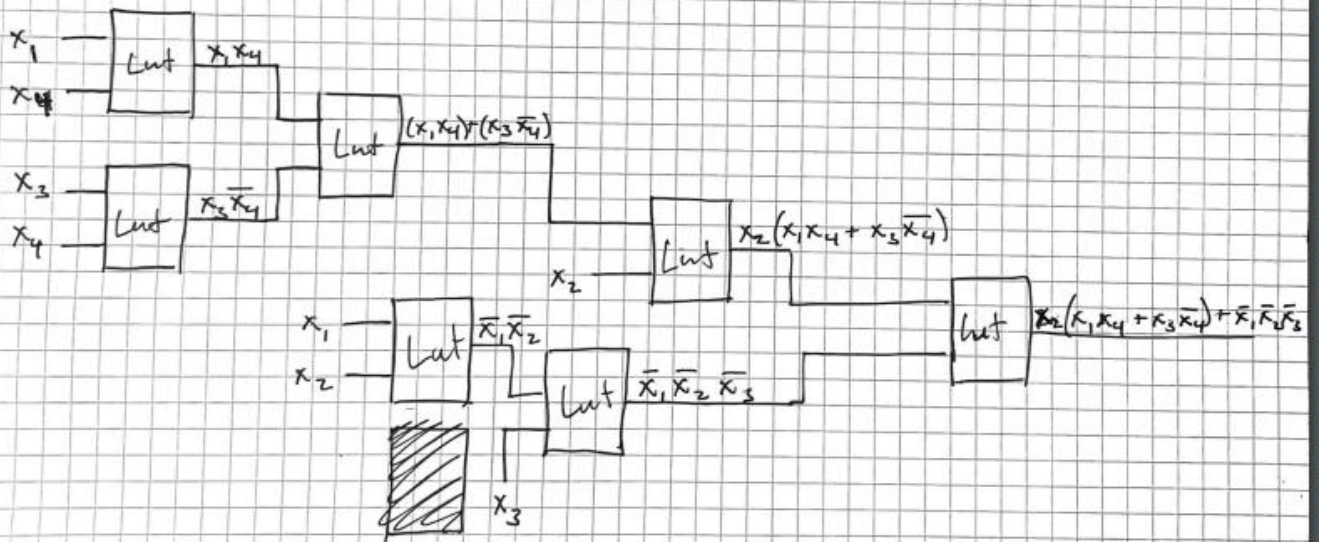
$$f = x_1 x_2 x_4 + x_2 x_3 \bar{x}_4 + \bar{x}_1 \bar{x}_2 \bar{x}_3 \rightarrow x_2(x_1 x_4 + x_3 \bar{x}_4) + \bar{x}_1 \bar{x}_2 \bar{x}_3$$



## Exercise 4

 

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity Hw6Q4SevenSegSolnTB is
end Hw6Q4SevenSegSolnTB;
```

```
architecture tb of Hw6Q4SevenSegSolnTB is
    signal bin : std_logic_vector (3 downto 0) := (others => '0');
    signal leds : std_logic_vector (1 to 7);
```

```
-- using unconstrained vectors in record
```

```
-- sized determined in constant
```

```
-- VHDL 2008 required
```

```
type test_rec is record
```

```
    bin : std_logic_vector;
```

```
    leds : std_logic_vector;
```

```
end record test_rec;
```

```
type test_rec_array is array (integer range <>) of test_rec;
```

```
constant test : test_rec_array := (
```

```
    ("0000", 7UX"7E"),
```

```
    ("0001", 7UX"30"),
```

```
    ("0010", 7UX"6D"),
```

```
    ("0011", 7UX"79"),
```

```
    ("0100", 7UX"33"),
```

```
    ("0101", 7UX"5B"),
```

```
    ("0110", 7UX"5F"),
```

```
    ("0111", 7UX"70"),
```

```
    ("1000", 7UX"7F"),
```

```
    ("1001", 7UX"7B"),
```

```
    ("1010", 7UX"77"),
```

```
    ("1011", 7UX"1F"),
```

```

        ("1100", 7UX"4E"),
        ("1101", 7UX"3D"),
        ("1110", 7UX"4F"),
        ("1111", 7UX"47")
    );
begin

    dut : entity work.seven_segment_decoder
    port map (bin => bin, leds => leds);

    stimuli : process
    begin
        for i in test'range loop
            bin <= test(i).bin;
            wait for 10 ns;
            assert leds = test(i).leds report "bin = " & to_hstring(bin) & " leds = " & to_hstring(leds) severity
note;
            end loop;
            wait;
        end process;

    end tb;

```

```

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

```

```

entity seven_segment_decoder is
port(
    bin : in std_logic_vector(3 downto 0);
    leds : out std_logic_vector(6 downto 0)
);
end seven_segment_decoder;

```


```

architecture Behavioral of seven_segment_decoder is
begin
    leds <= "1111110" when bin = "0000" else
        "0110000" when bin = "0001" else
        "1101101" when bin = "0010" else
        "1111001" when bin = "0011" else
        "0110011" when bin = "0100" else
        "1011011" when bin = "0101" else
        "1011111" when bin = "0110" else
        "1110000" when bin = "0111" else
        "1111111" when bin = "1000" else
        "1111011" when bin = "1001" else

```

```
"1110111" when bin = "1010" else  
"0011111" when bin = "1011" else  
"1001110" when bin = "1100" else  
"0111101" when bin = "1101" else  
"1001111" when bin = "1110" else  
"1000111" when bin = "1111" else  
"1111111";  
end Behavioral;
```

## Exercise 5

 

```
library ieee;
use ieee.std_logic_1164.ALL;
use ieee.numeric_std.all;
```

```
entity Hw6Q5Mux is
  port (
    shift_amt: in std_logic_vector(2 downto 0);
    y: out std_logic_vector(15 downto 0)
  );
end Hw6Q5Mux;
```

```
architecture oh_behavior of Hw6Q5Mux is
  -- create an array of vectors to hold each of the shifters
  type shifty_array is array (7 downto 0) of std_logic_vector(15 downto 0);
  signal y_array: shifty_array := (x"89AB", x"789A", x"6789", x"5678", x"4567", x"3456", x"2345",
x"1234");
begin
  y <= y_array(to_integer(unsigned(shift_amt)));
end oh_behavior;
```

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity Hw6Q5MuxTB is
end Hw6Q5MuxTB;
```

```
architecture tb of Hw6Q5MuxTB is
  signal shift_amt : std_logic_vector(2 downto 0) := (others => '0');
  signal y : std_logic_vector(15 downto 0);

  -- this record is constrained
  -- the index ranges are given
  type test_rec is record
    shift_amt : std_logic_vector(2 downto 0);
    y : std_logic_vector(15 downto 0);
  end record test_rec;
```



```

type test_rec_array is array(7 downto 0) of test_rec;
constant test : test_rec_array := (
    ("000", X"1234"),
    ("001", X"2345"),
    ("010", X"3456"),
    ("011", X"4567"),
    ("100", X"5678"),
    ("101", X"6789"),
    ("110", X"789A"),
    ("111", X"89AB")
);
begin

    dut : entity work.Hw6Q5Mux
        port map (shift_amt => shift_amt, y => y);

    stimuli : process
    begin
        for i in test'range loop
            shift_amt <= test(i).shift_amt;
            wait for 10 ns;
            assert (test(i).y = y) report "error in result. y is " &
                to_hstring(y) & " and should be = " &
                to_hstring(test(i).y) & " when the shift amount is = " &
                to_hstring(test(i).shift_amt);
            wait for 10 ns;
        end loop;
        wait;
    end process;

end tb;

```